01/05/2020

Project Aim

To build a device thats prevents reception of signals to Mobile phones

Project description:

This is a very simple and basic circuit and no programming is done

Hardwares to be used: Antenna, Transistors, Inductors, Resistors, Capacitors

Approach: Connect the components like given in the circuit diagram below and the jammer is ready

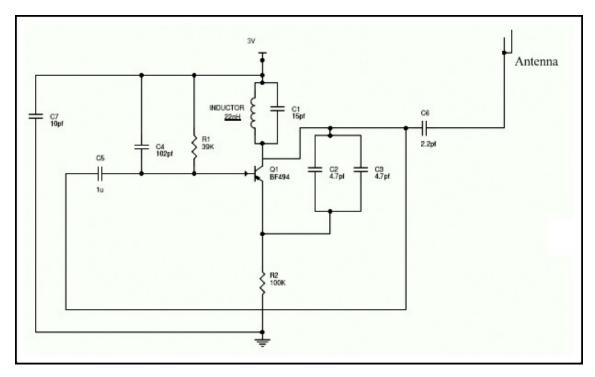


Figure 1: Circuit Diagram

ElectronicsClub Page 1